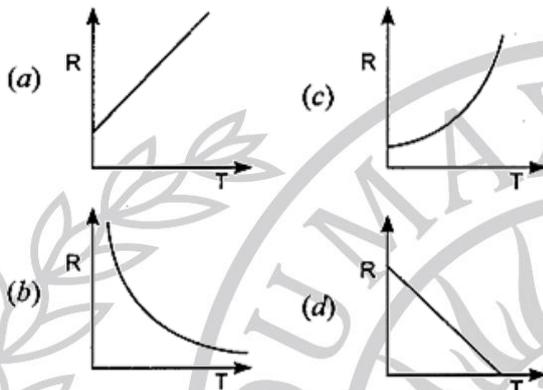



Practice sheet 2

- Each question carry 1 marks and time given for each is 2 min.
- All questions are compulsory.

1. A wire of length l , made of material resistivity ρ is cut into two equal parts. The resistivity of the two parts are equal to,
 - (a) ρ
 - (b) $1/\rho$
 - (c) 2ρ
 - (d) 4ρ
2. The temperature of a conductor is increased. The graph best showing the variation of its resistance is



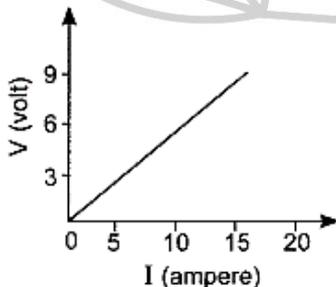3. A battery of 10 volt carries 20,000 C of charge through a resistance of 20 Ω . The work done in 10 seconds is
 - (a) 2×10^3 joule
 - (b) 2×10^5 joule
 - (c) 2×10^4 joule
 - (d) 2×10^2 joule
4. A boy records that 4000 joule of work is required to transfer 10 coulomb of charge between two points of a resistor of 50 Ω . The current passing through it is
 - (a) 2 A
 - (b) 4 A
 - (c) 8 A
 - (d) 16 A
5. The resistance whose V-I graph is given below is




- (a) $\frac{5}{3} \Omega$
- (b) $\frac{3}{5} \Omega$
- (c) $\frac{5}{2} \Omega$
- (d) $\frac{2}{5} \Omega$

6. Two wires of same length and area made of two materials of resistivity ρ_1 and ρ_2 are


connected in series to a source of potential V. The equivalent resistivity for the same area is

- (a) $\rho_1 + \rho_2$
- (b) $\frac{\rho_1 \rho_2}{\rho_1 + \rho_2}$
- (c) $\frac{(\rho_1 + \rho_2)}{\rho_1 \rho_2}$
- (d) $\left(\frac{|\rho_1 + \rho_2|}{2} \right)$


7. Two devices are connected between two points say A and B in parallel. The physical quantity that will remain the same between the two points is
 - (a) current
 - (b) voltage
 - (c) resistance
 - (d) None of these
8. Two wires of same length and area, made of two materials of resistivity ρ_1 and ρ_2 are connected in parallel V to a source of potential. The equivalent resistivity for the same length and area is
 - (a) $\rho_1 + \rho_2$
 - (b) $\frac{\rho_1 \rho_2}{\rho_1 + \rho_2}$
 - (c) $\frac{(\rho_1 + \rho_2)}{\rho_1 \rho_2}$
 - (d) $|\rho_1 - \rho_2|$
9. Calculate the current flows through the 10 Ω resistor in the following circuit.

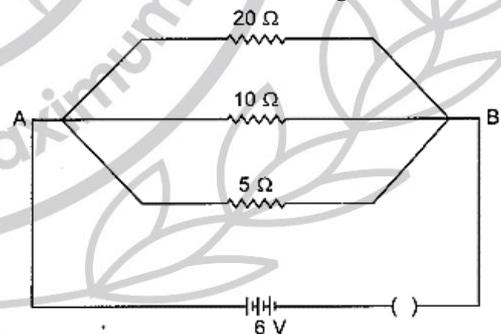

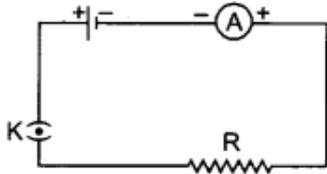
- (a) 1.2 A
- (b) 0.6 A
- (c) 0.2 A
- (d) 2.0 A
10. Two resistors are connected in series gives an equivalent resistance of 10 Ω . When connected in parallel, gives 2.4 Ω . Then the individual resistance are
 - (a) each of 5 Ω
 - (b) 6 Ω and 4 Ω
 - (c) 7 Ω and 4 Ω
 - (d) 8 Ω and 2 Ω
11. A cell, a resistor, a key, and an ammeter are arranged as shown in the circuit diagrams.



(i)

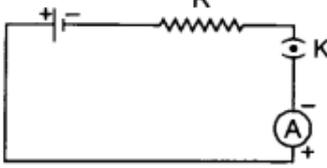

(ii)

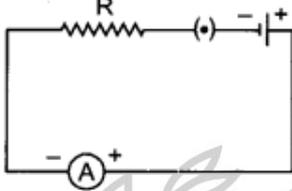

(iii)


The current recorded in the ammeter will be

- (a) maximum in (i)
- (b) maximum in (ii)
- (c) maximum in (iii)
- (d) same in all the cases

12. A current of 1 A is drawn by a filament of an electric bulb. Number of electrons passing through a cross-section of the filament in 16 seconds would be roughly
- (a) 10^{20}
 - (b) 10^{16}
 - (c) 10^{18}
 - (d) 10^{23}

13. A cylindrical conductor of length l and uniform area of cross-section A has resistance R . Another conductor of length $2l$ and resistance R of the same material has area of cross-section
- (a) $A/2$
 - (b) $3A/2$
 - (c) $2A$
 - (d) $3A$

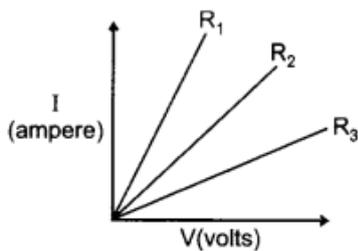14. A student carries out an experiment and plots the V-I graph of three samples of nichrome wire with resistances R_1 , R_2 and R_3 respectively. Which of the following is true?



- (a) $R_1 = R_2 = R_3$
- (b) $R_1 > R_2 > R_3$
- (c) $R_3 > R_2 > R_1$
- (d) $R_2 > R_3 > R_1$

15. The resistivity does not change if

- (a) the material is changed
- (b) the temperature is changed
- (c) the shape of the resistor is changed
- (d) both material and temperature are changed

16. Electric potential is a:

- (a) scalar quantity
- (b) vector quantity
- (c) neither scalar nor vector
- (d) sometimes scalar and sometimes vector

17. 1 mV is equal to:

- (a) 10 volt
- (b) 1000 volt
- (c) 10^{-3} volt
- (d) 10^{-6} volt

18. Coulomb is the SI unit of:

- (a) charge
- (b) current
- (c) potential difference
- (d) resistance

19. When electric current is passed, electrons move from:

- (a) high potential to low potential.
- (b) low potential to high potential.
- (c) in the direction of the current.
- (d) against the direction of the current.

20. The electrical resistance of insulators is

- (a) high
- (b) low
- (c) zero
- (d) infinitely high

21. Electrical resistivity of any given metallic wire depends upon

- (a) its thickness
- (b) its shape
- (c) nature of the material
- (d) its length

22. Which of the following is not correctly matched?

- (a) : An electric cell
- (b) : A resistor
- (c) : Open plug key

23. The resistivity of insulators is of the order of

- (a) $10^{-8} \Omega\text{-m}$
- (b) $10^1 \Omega\text{-m}$
- (c) $10^{-6} \Omega\text{-m}$
- (d) $10^6 \Omega\text{-m}$

24. Which of the following gases are filled in electric bulbs?

- (a) Helium and Neon
- (b) Neon and Argon
- (c) Argon and Hydrogen
- (d) Argon and Nitrogen

25. 100 J of heat is produced each second in a 4Ω resistor. The potential difference across the resistor will be:

- (a) 30 V
- (b) 10 V
- (c) 20 V
- (d) 25 V